

# **IA LAB: Ladder Logic Programmes**

Student name: *Darsh Gajjar*

---


Course: *Industrial Automation LAB* – Professor: *Dr. H. G. Patel*  
Due date: *04/01/2021*

### Program #1

There is Big godown in which there are 3 sensors installed,

- If any one sensor is on then indicators ON,
- If any two sensors on then hooters ON,
- If all sensors are ON then Fire extinguisher should be ON

**Answer.**

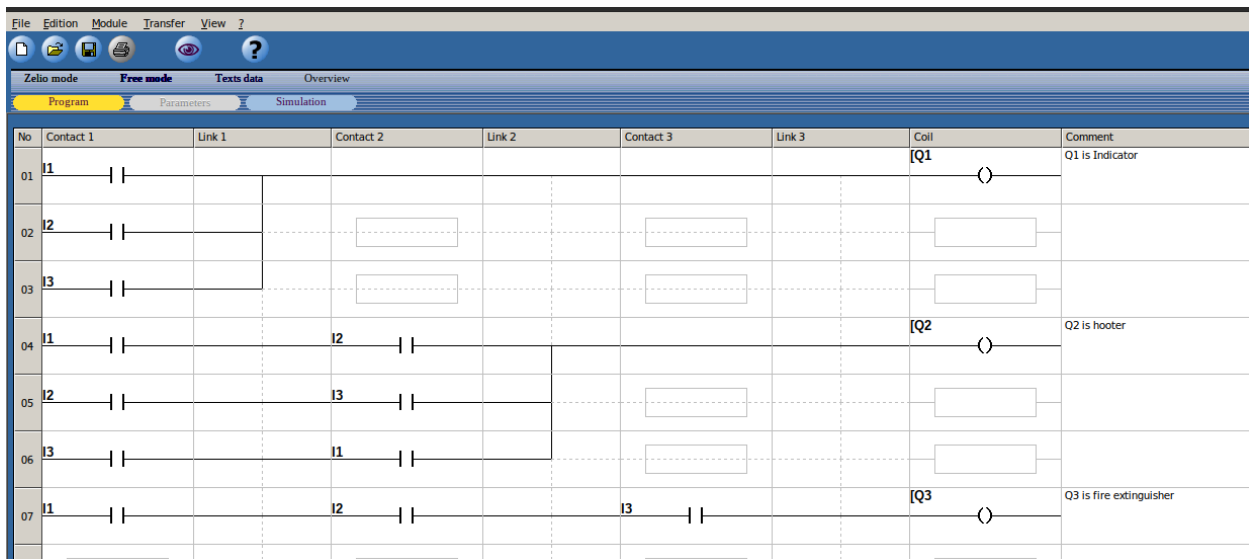


### Program #2

One cutting machine with left and right start switches

- If both switches on then machine on
- When you release any switch machine off

**Answer.**

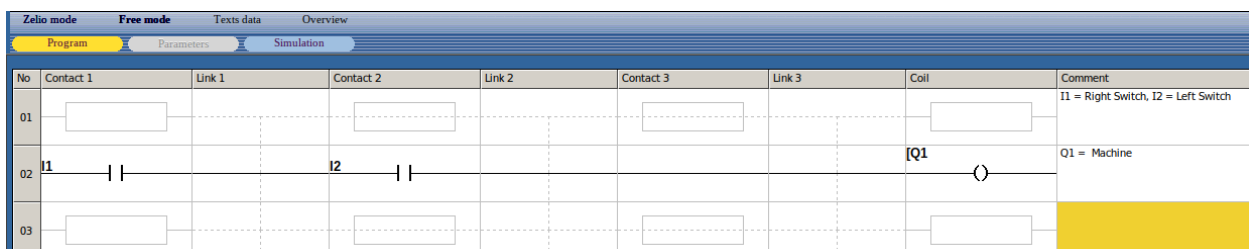

### Program #3

whenever we press ON Push button then Motor should remain ON and when STOP push button is press it should OFF immediately

**Answer.**

| Zelio entry   Ladder entry   Configuration   Text entry |           |           |           |           |           |      |                                    |
|---------------------------------------------------------|-----------|-----------|-----------|-----------|-----------|------|------------------------------------|
| No                                                      | Contact 1 | Contact 2 | Contact 3 | Contact 4 | Contact 5 | Coil | Comment                            |
| 001                                                     | I1        |           | I2        |           |           | Q1   | I1 = Start , I2 = Stop, Q1 = Motor |
| 002                                                     | Q1        |           |           |           |           |      |                                    |

**Program #4**

In 35 feet long machine design ladder logic by which operator should able to Start and Stop from three different place

**Answer.**

| Zelio entry   Ladder entry   Configuration   Text entry |           |           |           |           |           |      |                                                  |
|---------------------------------------------------------|-----------|-----------|-----------|-----------|-----------|------|--------------------------------------------------|
| No                                                      | Contact 1 | Contact 2 | Contact 3 | Contact 4 | Contact 5 | Coil | Comment                                          |
| 001                                                     | I1        | I5        | I4        | I6        |           | Q1   | Q1 = Machine , I1,I2,I3 = Start, I4,I5,I6 = Stop |
| 002                                                     | I2        |           |           |           |           |      |                                                  |
| 003                                                     | I3        |           |           |           |           |      |                                                  |
| 004                                                     | Q1        |           |           |           |           |      |                                                  |

**Program #5**

There is one lubrication Pump and one Motor

- first lubrication Pump should be On and then Motor ON
- When STOP Push button is pressed Motor and Pump should be Stop together


**Answer.**

| Zelio entry   Ladder entry   Configuration   Text entry |           |           |           |           |           |      |                                             |
|---------------------------------------------------------|-----------|-----------|-----------|-----------|-----------|------|---------------------------------------------|
| No                                                      | Contact 1 | Contact 2 | Contact 3 | Contact 4 | Contact 5 | Coil | Comment                                     |
| 001                                                     | I1        | I2        |           |           |           | Q1   | Q1 = Lubrication Pump, I1 = Start, I2= Stop |
| 002                                                     | Q1        |           |           |           |           |      |                                             |
| 003                                                     | Q1        |           |           |           |           | Q2   | Q2 = Motor                                  |
| 004                                                     |           |           |           |           |           |      |                                             |

**Program #6**

One 3-phase Induction Motor need to operate in forward /reverse direction when motor start operate in forward direction reverse direction should off first and when operate in reverse direction then forward direction should off first


**Answer.**

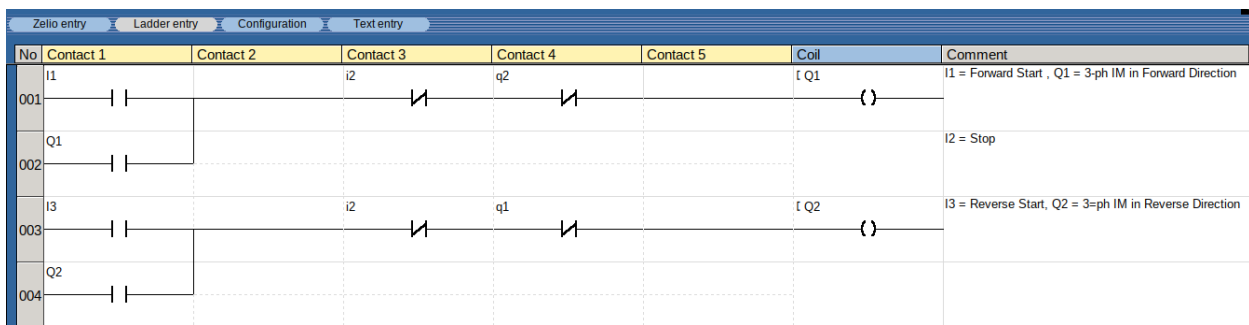

### Program #7

There is one motor and one pump, when start push button is pressed first pump and afterward motor should start and STOP button is individual.

**Answer.**

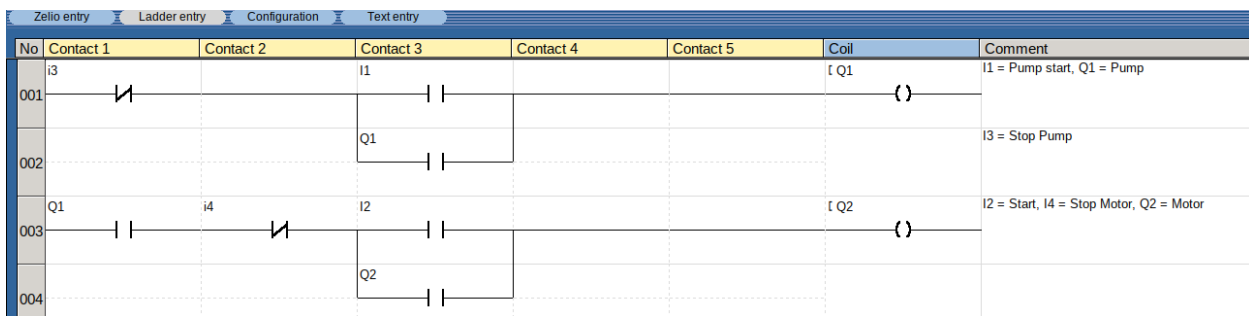


### Program #8



There are two Motors, in which one should work at one time and other remains in standby

1. with Stop Push button
2. with Set/reset coils
3. without any STOP push button

**Answer.**

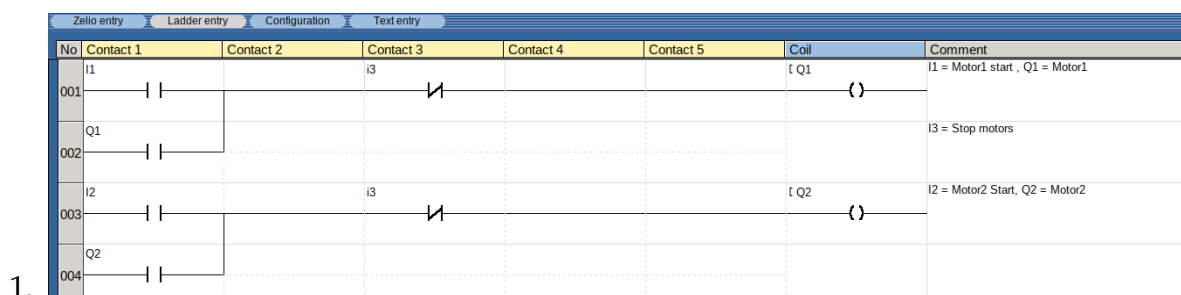

1.

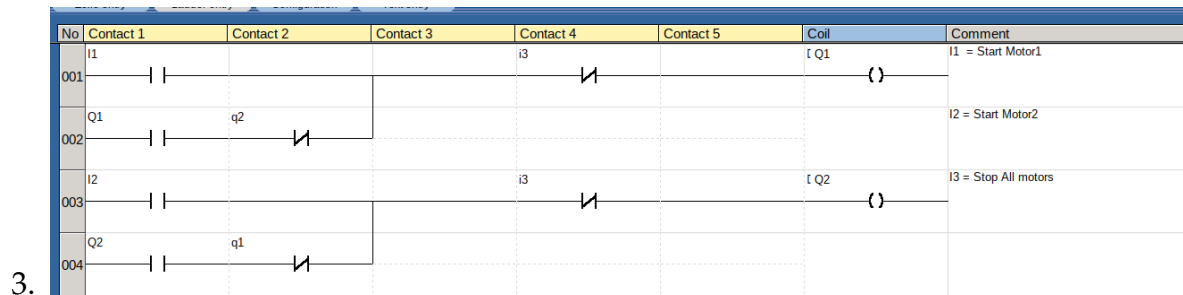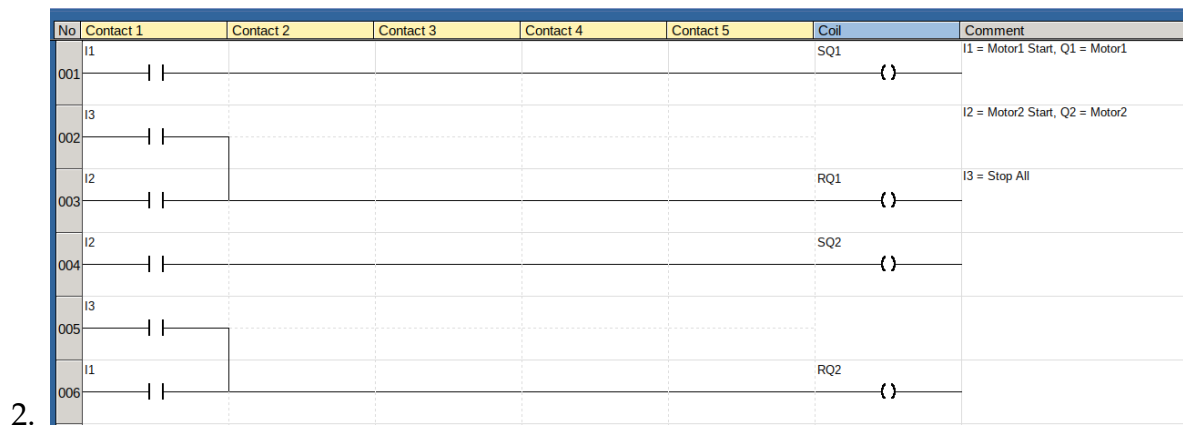


### Program #09

There are two motors

- start motor1, after 10 second motor2 start automatically
- when motor1 stops second one stops automatically

**Answer.**

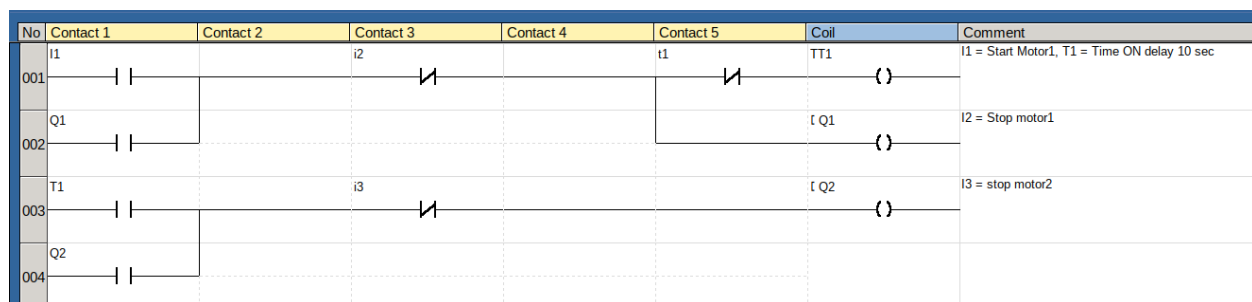

### Program #10

There are three motors

- when start push button is pressed Motor1 ON
- after 5 sec Motor2 ON
- after 5 sec Motor3 ON
- when STOP push button is pressed all should STOP together

**Answer.**

| No  | Contact 1 | Contact 2 | Contact 3 | Contact 4 | Contact 5 | Coil | Comment                             |
|-----|-----------|-----------|-----------|-----------|-----------|------|-------------------------------------|
| 001 | I1        |           |           |           | t1        | TT1  | I1 = Start , I2 = Stop              |
| 002 | Q1        |           |           |           | i2        | I Q1 | T1, T2, T3 = Time ON delay of 5 sec |
| 003 | T1        |           |           |           | t2        | TT2  |                                     |
| 004 | Q2        |           |           |           | i2        | I Q2 |                                     |
| 005 | T2        |           |           |           | i2        | I Q3 |                                     |
| 006 | Q3        |           |           |           |           |      |                                     |

### Program #11

There are two motors

- when start push button is pressed Motor1 ON and then after 5 second Motor2 ON
- when stop push button is pressed Motor1 off and then after 5 second Motor2 Off

**Answer.**

| No  | Contact 1 | Contact 2 | Contact 3 | Contact 4 | Contact 5 | Coil | Comment                 |
|-----|-----------|-----------|-----------|-----------|-----------|------|-------------------------|
| 001 | I1        |           |           |           | t1        | TT1  | I1 = Start , I2 = Stop  |
| 002 | Q1        |           |           |           | i2        | I Q1 | T1, T2 = On delay Timer |
| 003 | T1        |           |           |           | t2        | I Q2 |                         |
| 004 | Q2        |           |           |           |           |      | M1 = memory coil bit    |
| 005 | I2        |           |           |           |           | TT2  |                         |
| 006 | M1        |           |           |           |           | I M1 |                         |

### Program #12

Consider one wood cutting machine and one blower as soon as wood cutting machine starts, blower should start, when wood cutting machine stops, blower stop after 10 second

**Answer.**

| No  | Contact 1 | Contact 2 | Contact 3 | Contact 4 | Contact 5 | Coil | Comment                                    |
|-----|-----------|-----------|-----------|-----------|-----------|------|--------------------------------------------|
| 001 | I1        | I2        |           |           |           | Q1   | I1 = Start Blower and Wood cutting machine |
| 002 | Q1        |           |           |           |           |      | Q1 = Wood cutting machine machine          |
| 003 | Q1        |           |           |           |           | TT1  | Q2 = Blower                                |
| 004 | T1        |           |           |           |           | Q2   | T1 = Off delay timer                       |

### Program #13

There are two motors


- Motor1 start immediately after Push button is pressed
- After 5 second Motor2 start and Motor1 Stop
- After 5 second Motor1 Start and Motor2 Stop

operate motors alternate mode continuously


1. Do above logic using set/reset coil bit and two timers
2. Do above logic using set/reset coil bit and one timer
3. Do above logic using without set/reset and two timers
4. Do above logic using without set/reset and One timer

**Answer.**


1. using set/reset and two timer

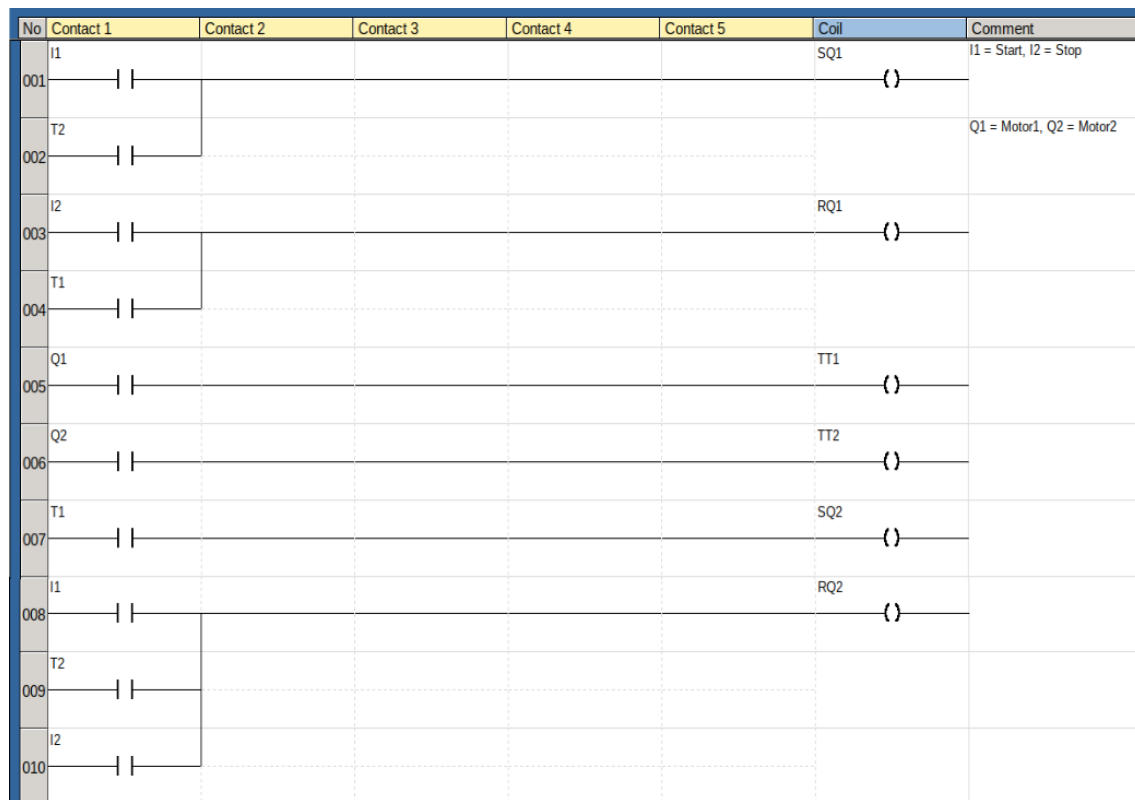

## 2. using set/reset and one timer

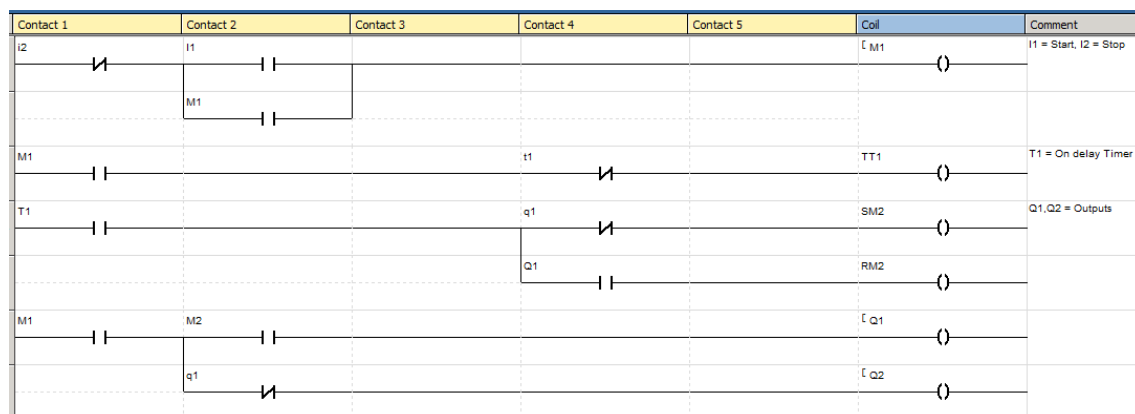


## 3. without set/reset and two timers

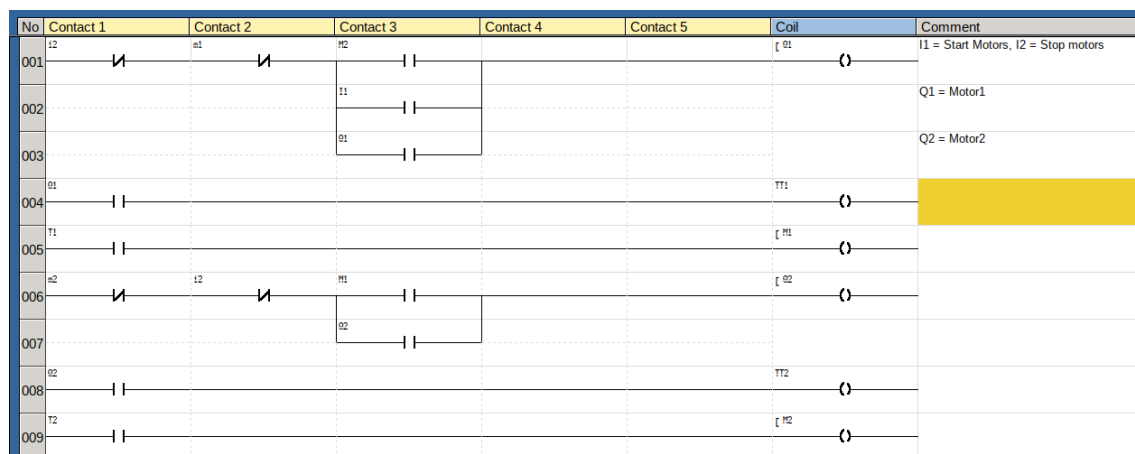




## 4. without set/reset and one timer

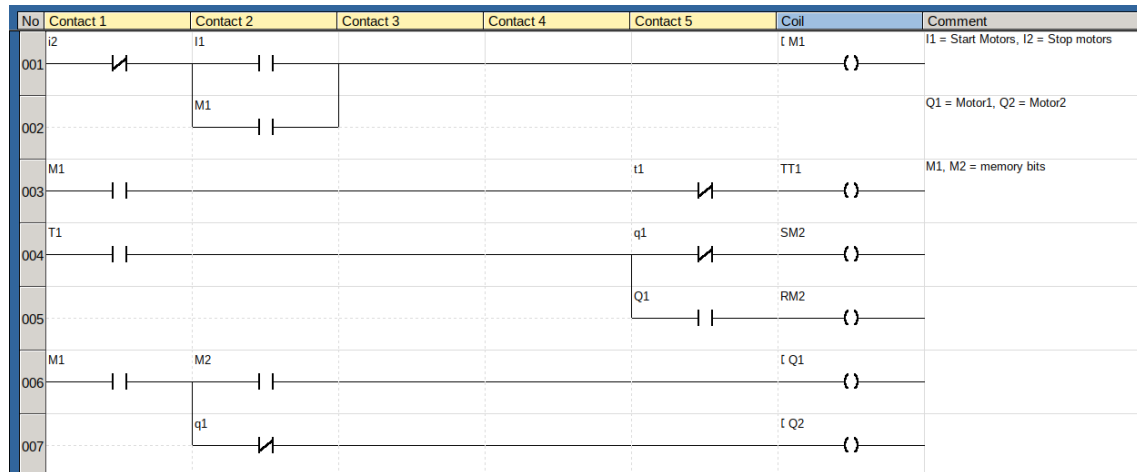**Program #14**

One motor is operate using single push button and then when button pressed first motor should be ON and when pressed same button again it should OFF, then again if button pressed it should start again.

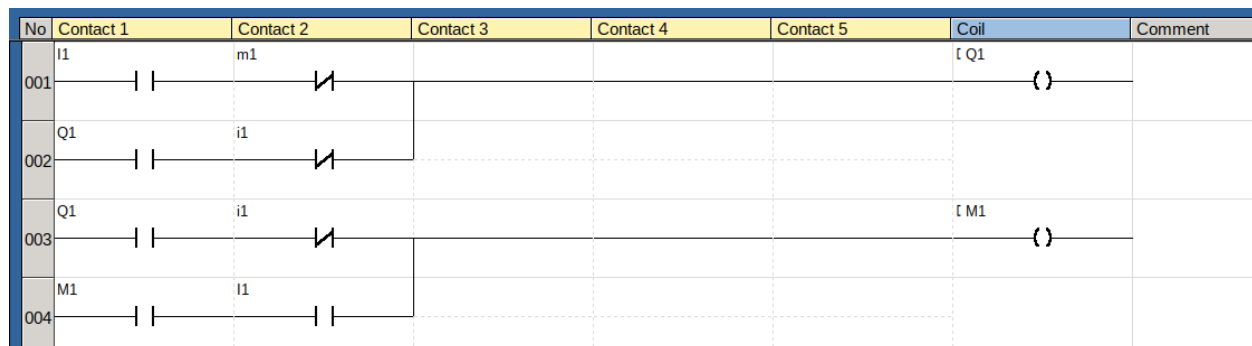
**Answer.****Program #15**

In One bottle filling plant, there are 6 bottles in each box


1. when six bottles are filled 1<sup>st</sup> indicator should be ON
2. when 5 such box are packed 2<sup>nd</sup> indicator should be ON

**Answer.**

1. answer of 1<sup>st</sup> part

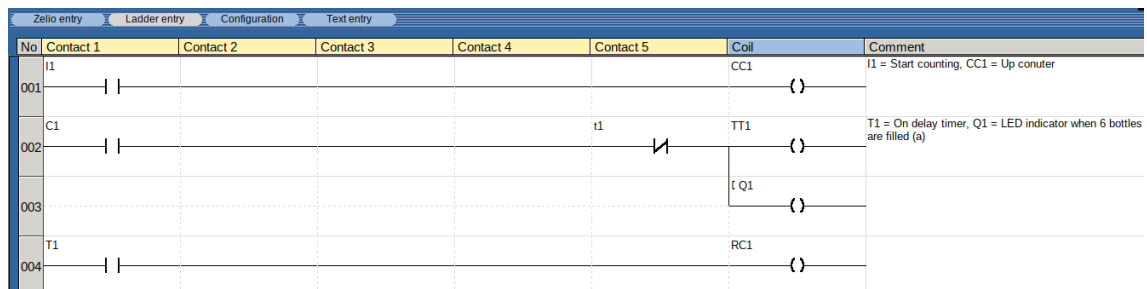


2. answer of 2<sup>nd</sup> part

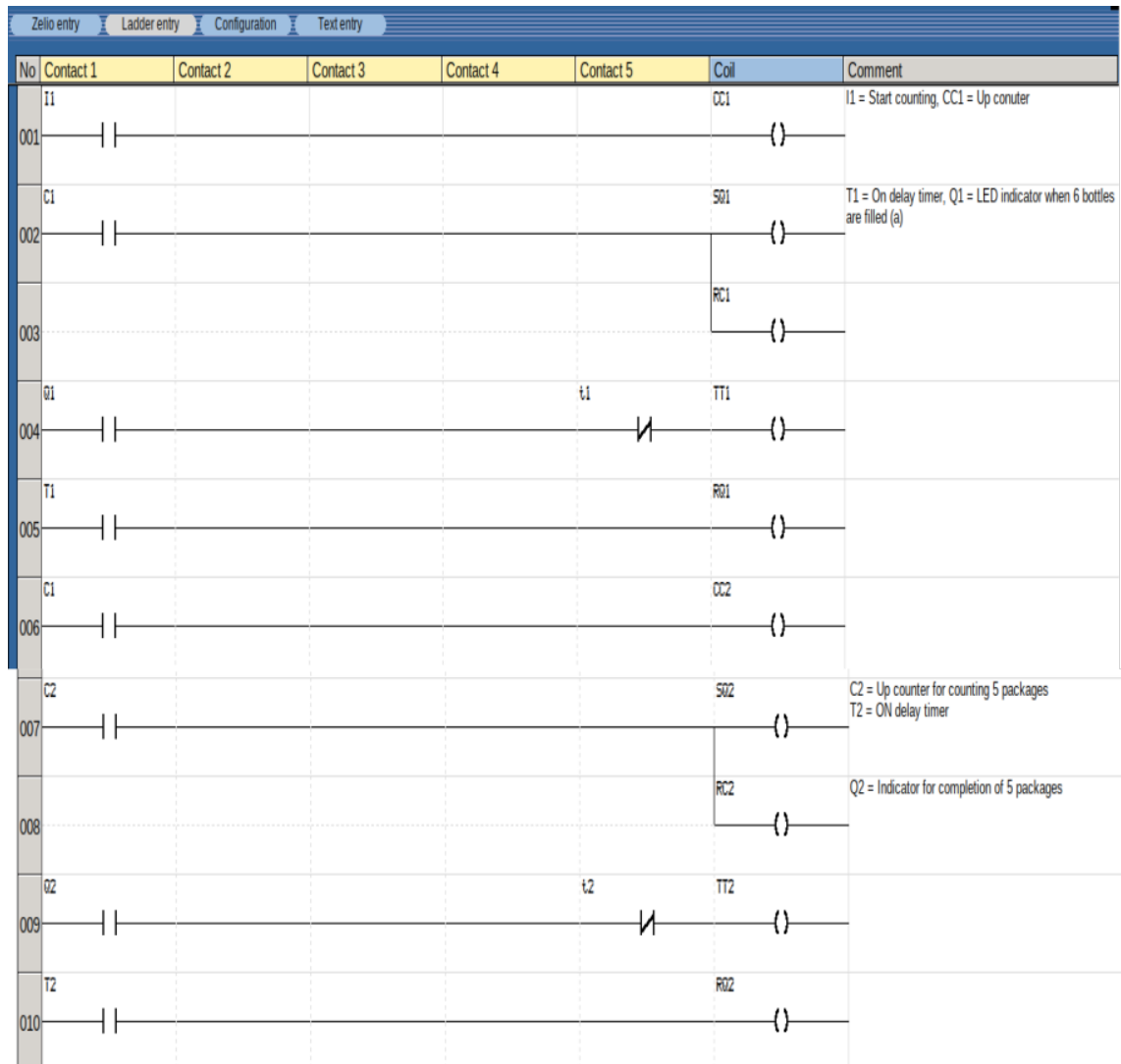


## Program #16

In Automatic blending process there are sequence of operations are going to held as per flowchart and design ladder logic for it.

Flow chart of problem 16

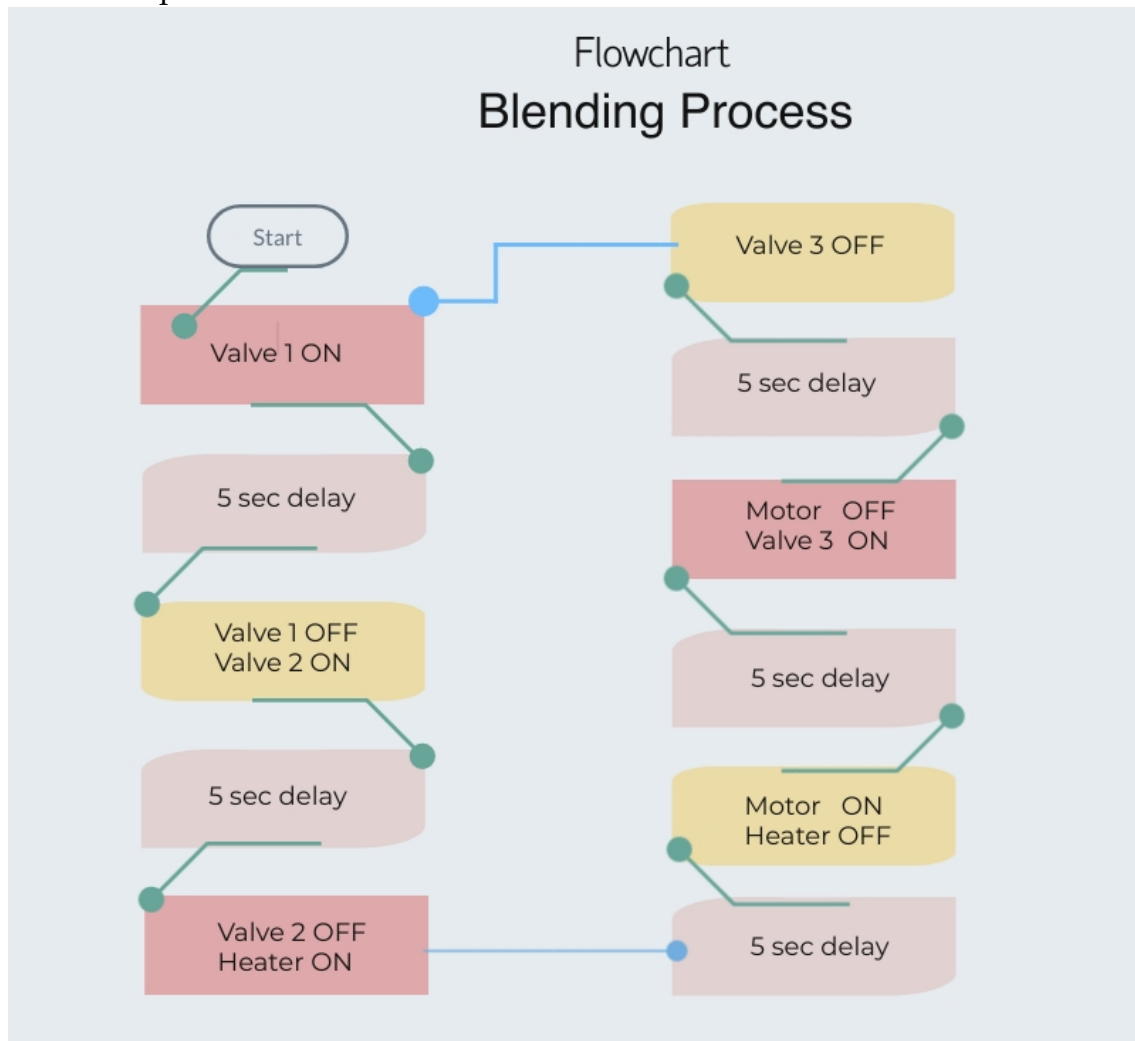

**Answer.**

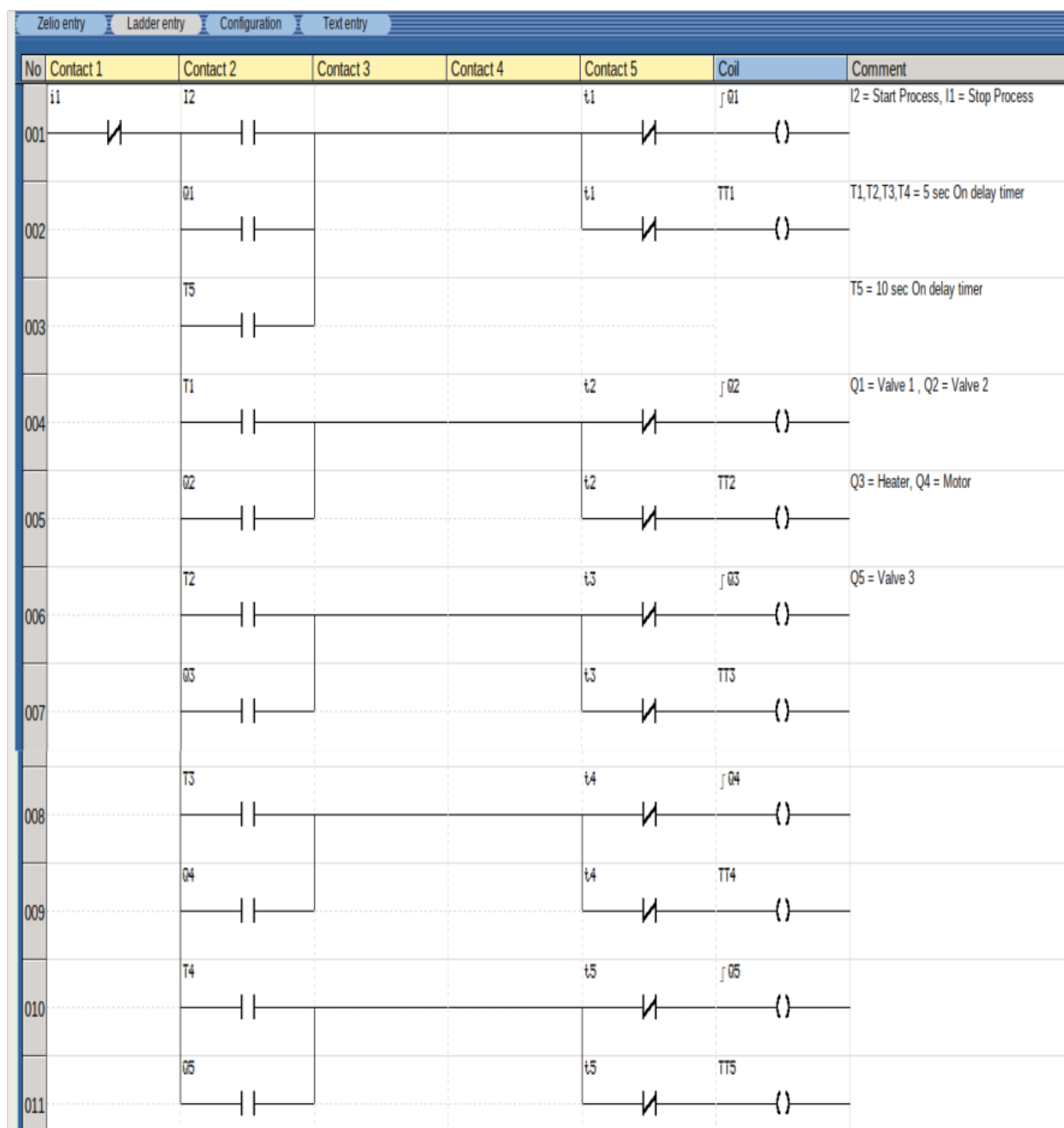


### Program #17

When Process start One Light blinking at varying frequency as stated below

- when 1<sup>st</sup> push button is pressed Light is On and OFF at every 1 second
- when 2<sup>nd</sup> push button is pressed Light is On and OFF at every 2 second
- when 3<sup>rd</sup> push button is pressed Light is On and OFF at every 3 second
- when 4<sup>th</sup> push button is pressed Light is flickering at 0.5 Hz frequency.

**Answer.**

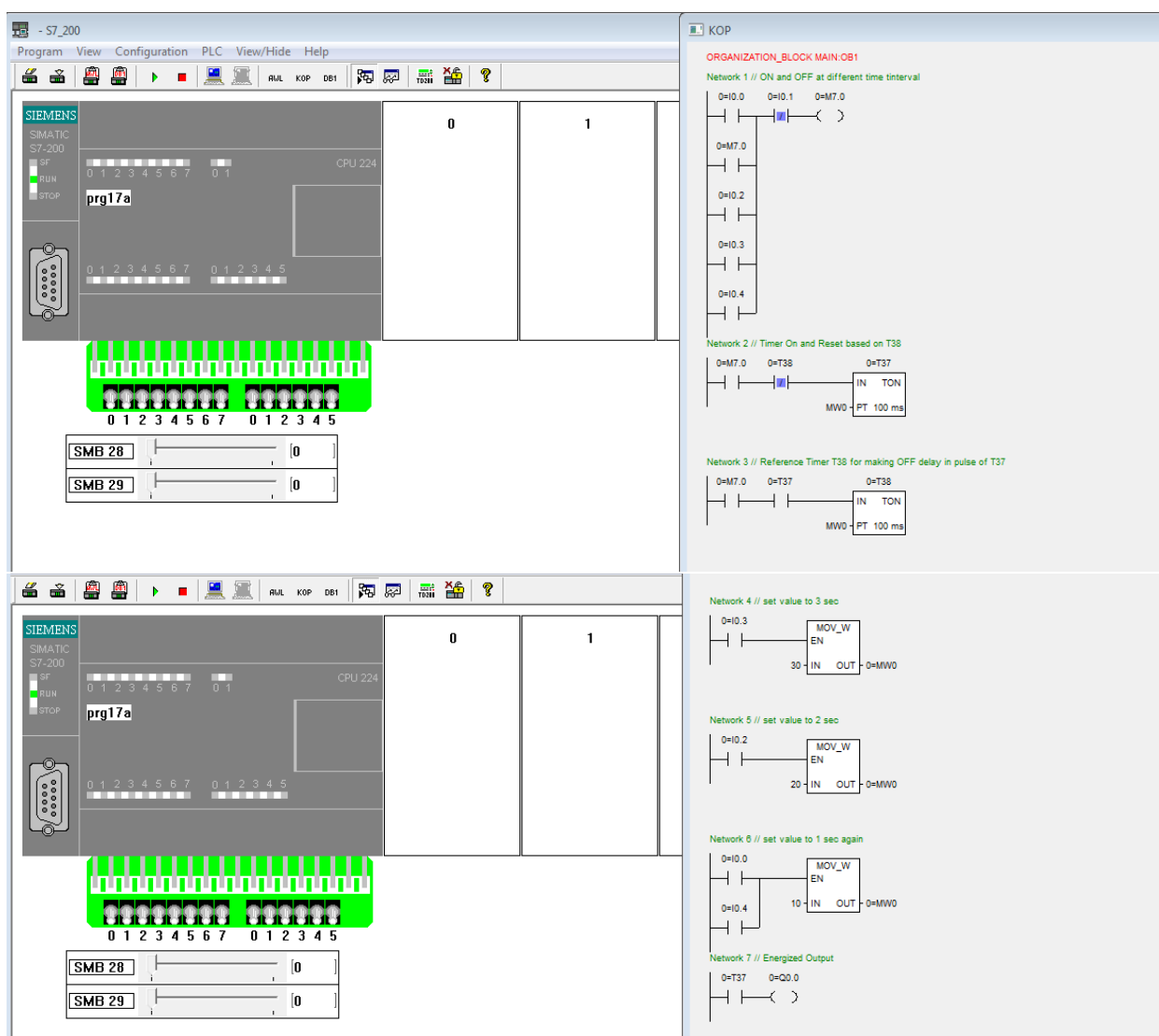

### Program #18

In one process when start PB is pressed Timer starts

- when Timer reach to 3 sec PUMP ON
- when Timer reach to 6 sec Motor ON
- when Timer reach to 7 sec Motor OFF
- when Timer reach to 8 sec PUMP OFF

Answer.




### Program #20

There are three no of motors, when Start PB is pressed Timer starts

- from time interval 0 to 10 sec Motor1 & Motor3 ON
- from time interval 10 to 20 sec Motor2 ON
- from time interval 20 to 30 sec Motor2 & Motor3 ON
- from time interval 30 to 40 sec All Motors ON
- when time in seconds > 40 sec All motors OFF


**Answer.**

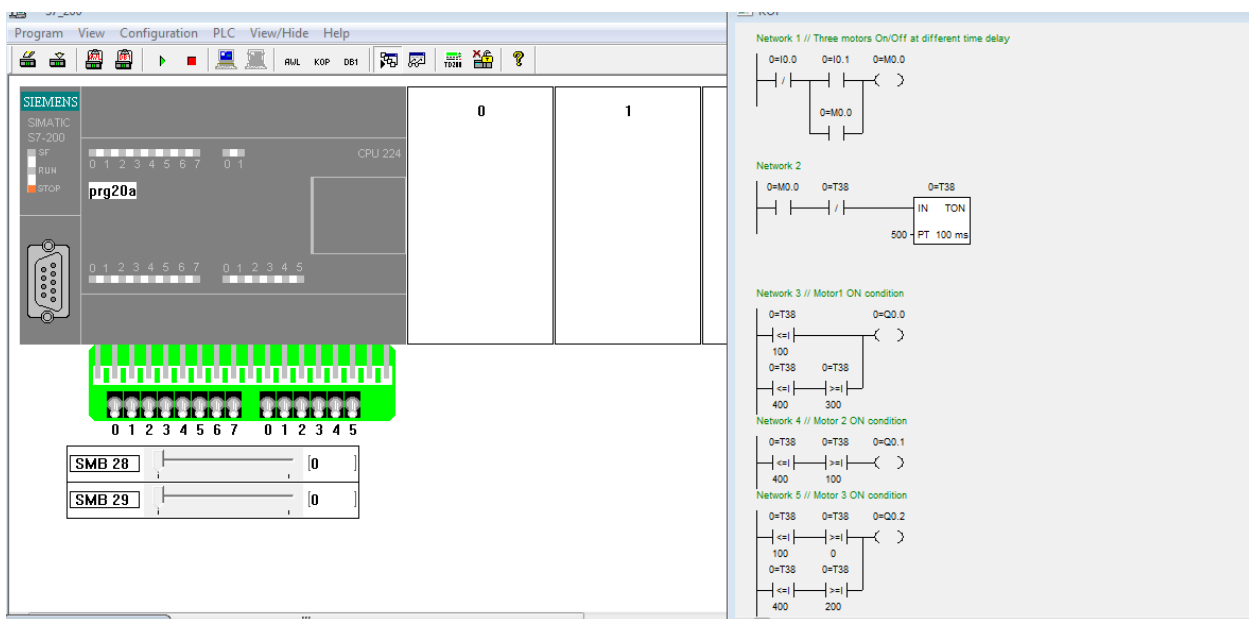

### Program #21

Convert data that stored in Byte into real data Or convert data into %VBXX into Real value.

**Answer.**

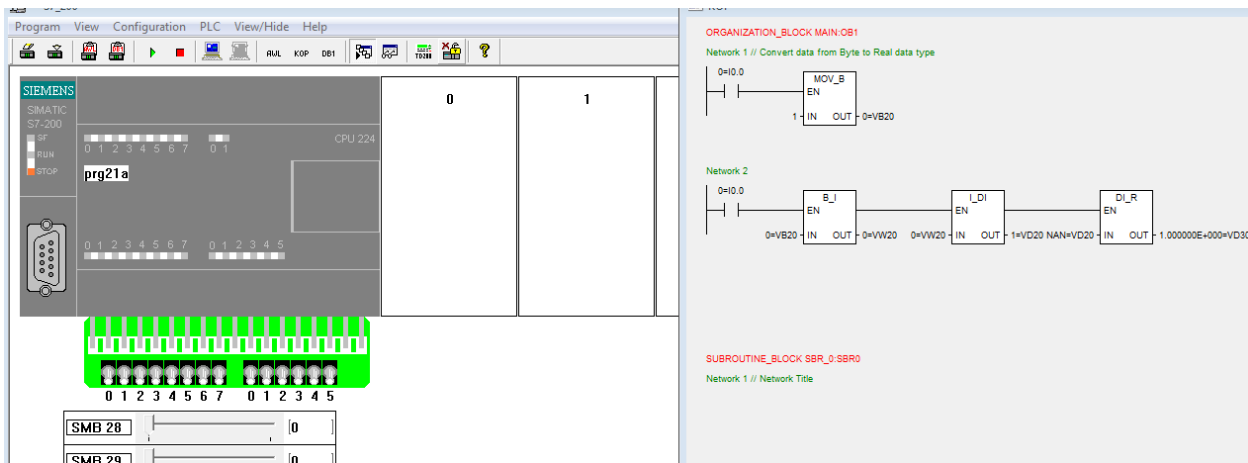


### Program #22

Design a programme in which there is input of data available from User/HMI

- if input data is  $\leq 255$  then convert it into byte data type and store into(%VBXX) and also energized one output.
- if input data is  $\leq 32000$  and  $\geq 256$  then convert it into integer data type and store into(%VWXX) and also energized two outputs.
- if input data is  $> 32000$ , then energized three outputs.

Answer.

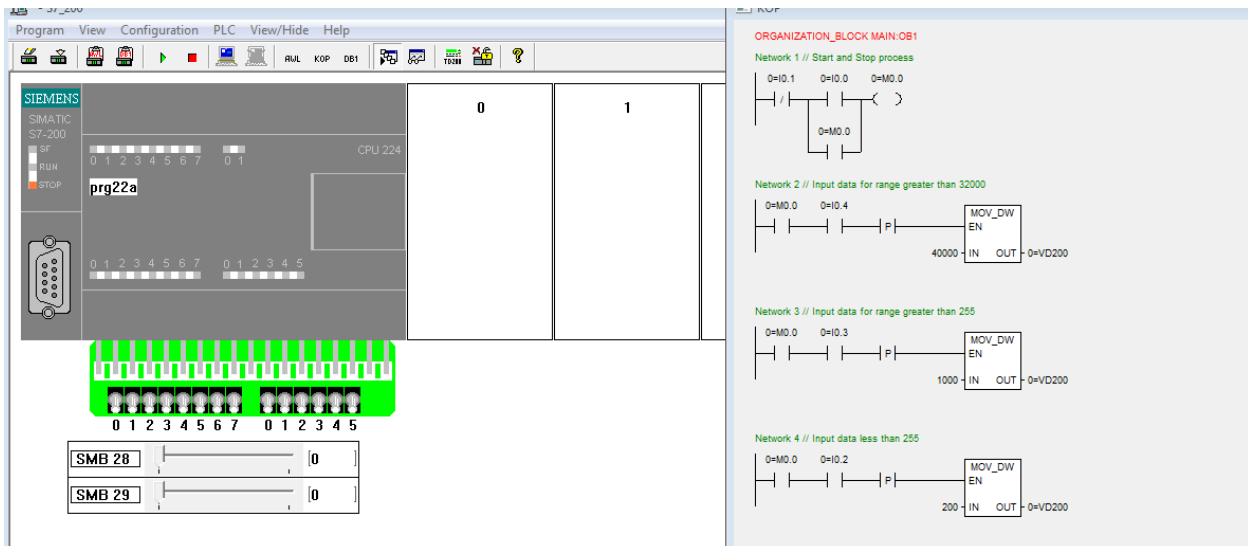



**Network 5 // condition for set memory coil**

```

0=M0.0 0=VD200 0=M0.1
|-----| D |-----|>
32000

```

**Network 6**

```

0=M0.0 0=VD200 0=VW50 0=M0.2
|-----|>D|-----|DI_L|-----|>=|
32000 0=VD200 IN OUT 0=VW50 255

```

**Network 7**

```

0=M0.0 0=VW50 0=VB100 0=M0.3
|-----|<=|-----|L_B|-----|>=|
255 0=VW50 IN OUT 0=VB100 1

```

**Network 8 // On at every condition hold true**

```

0=M0.1 0=Q0.0
|-----|>
0=M0.2
|-----|>

```

**Network 9 // this Output On for data less than 32000**

```

0=M0.1 0=Q0.1
|-----|>
0=M0.2
|-----|>

```

**Network 10 // this output On for data greater than 32000**

```

0=M0.1 0=Q0.2
|-----|>

```

**Network 11 // Reset all memory data with 0 values**

```

0=M0.1
|-----|P|-----|MOV_DW|
EN 0-IN OUT 0=VD200

```

**Network 10 // this output On for data greater than 32000**

```

0=M0.1 0=Q0.2
|-----|>

```

**Network 11 // Reset all memory data with 0 values**

```

0=M0.1
|-----|P|-----|MOV_DW|
EN 0-IN OUT 0=VD200
|-----|P|-----|MOV_W|
EN 0-IN OUT 0=VW50


```


**SUBROUTINE\_BLOCK SBR\_0.SBR0**

**Network 1 // Network Title**

When one Process starts: 1 light On and Off at one seconds(Current time interval = 2(1 sec ON + 1 sec OFF) sec)

- Answer.**

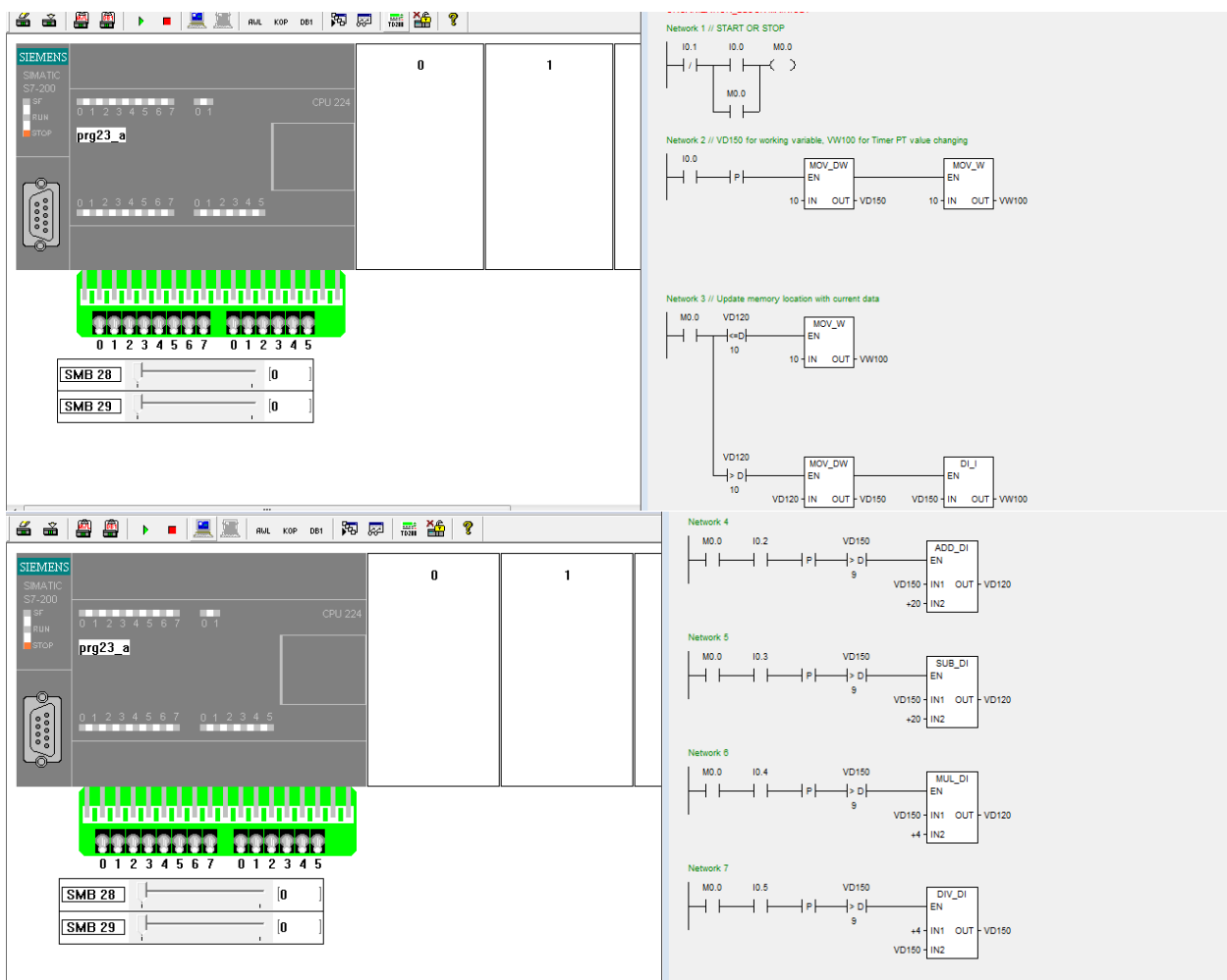

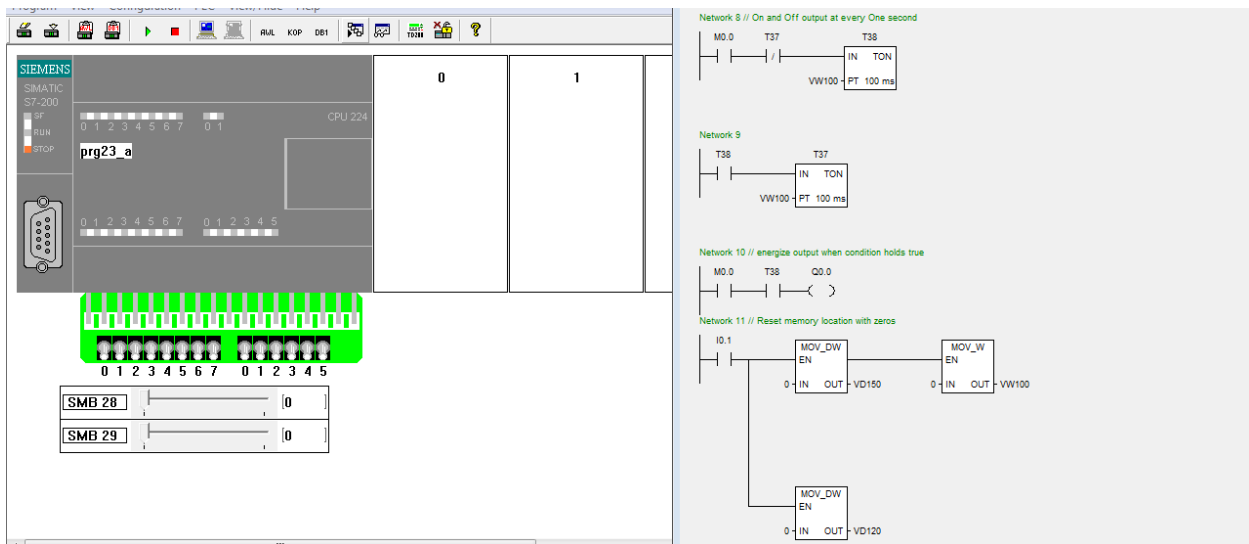



### Program #24

There are three heaters and one RTD sensor with transmitter connected with PLC.(eg PLC will read analog value in AIW0 From from 0 to 32000 counts) where  $0^{\circ}\text{C}$  to  $300^{\circ}\text{C}$  data transmit by interpolating with current signal of 4 to 20mA

- when temp is  $\lesssim 60^{\circ}$ , All three heaters ON
- when  $60 < \text{temp} \lesssim 150$ , any Two heaters will be ON
- when  $150 < \text{temp} \lesssim 250$ , Only one heater will be ON
- when  $\text{temp} > 250$ , All heaters should be OFF

Answer.

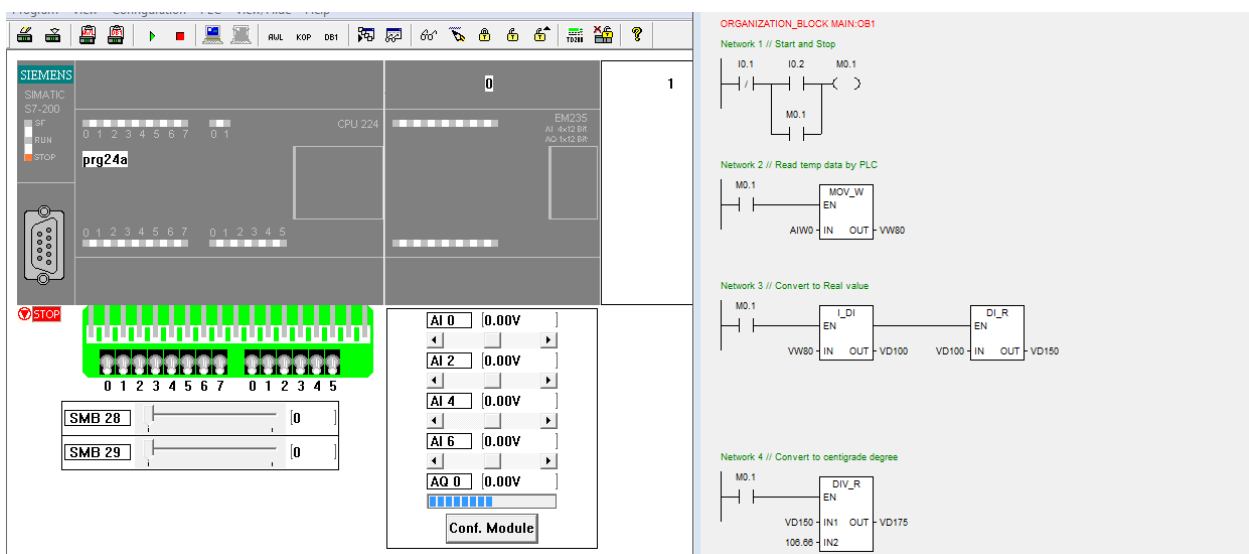

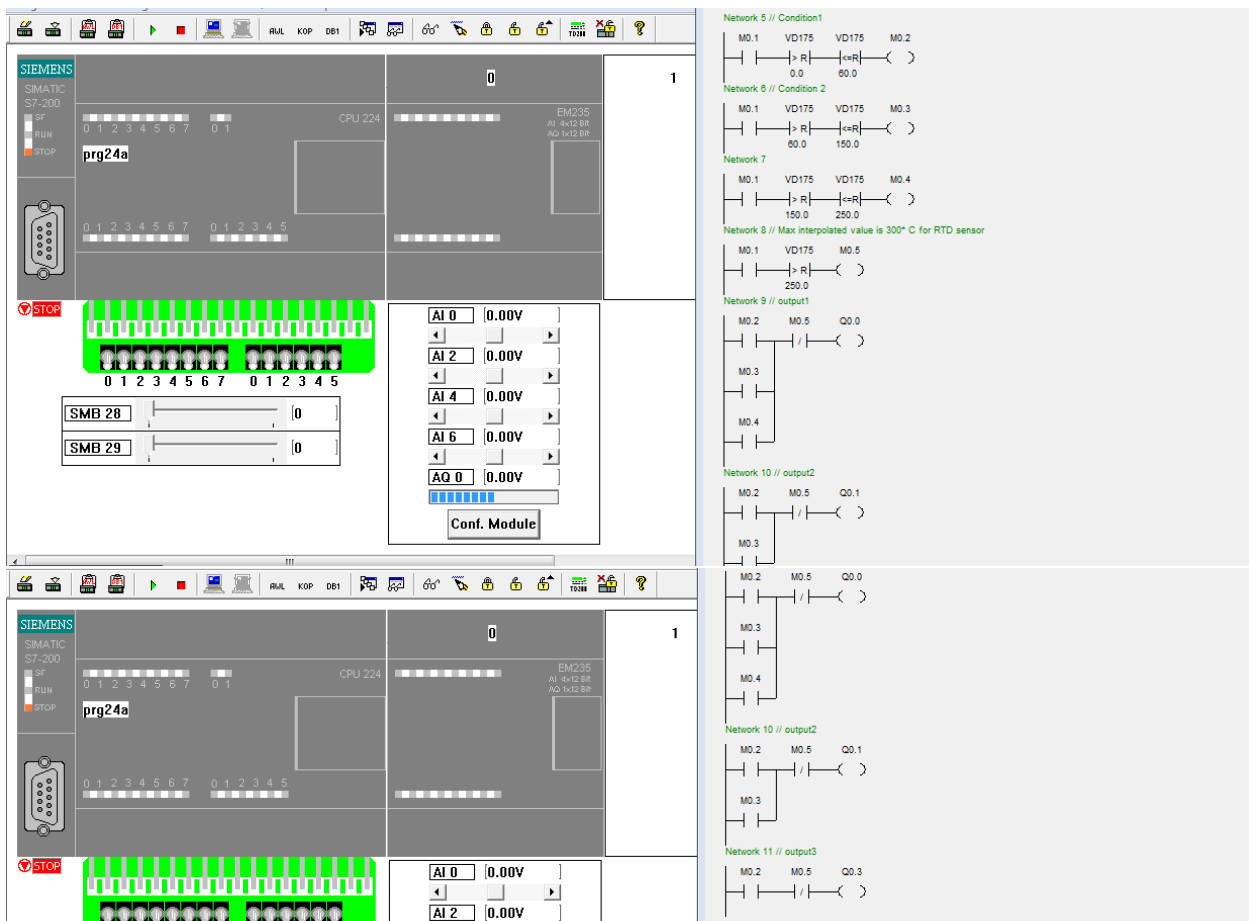


### Program #25


In a process, there are two sensors and 3 Outputs in which one is pressure sensor that is read value from 0 to 6 bar, and one temperature sensor use to control three heaters as per below condition.

- Process is start only if pressure is grater than 3 bar
- when temp is less than 50°C all heaters will be ON
- when  $50^{\circ}\text{C} < \text{temp} \lesssim 80^{\circ}\text{C}$  two heaeters will be ON
- when  $80^{\circ}\text{C} < \text{temp} \lesssim 150^{\circ}\text{C}$  only one heater will be ON
- when  $\text{temp} > 120^{\circ}\text{C}$  All heaters should be OFF


**Answer.**

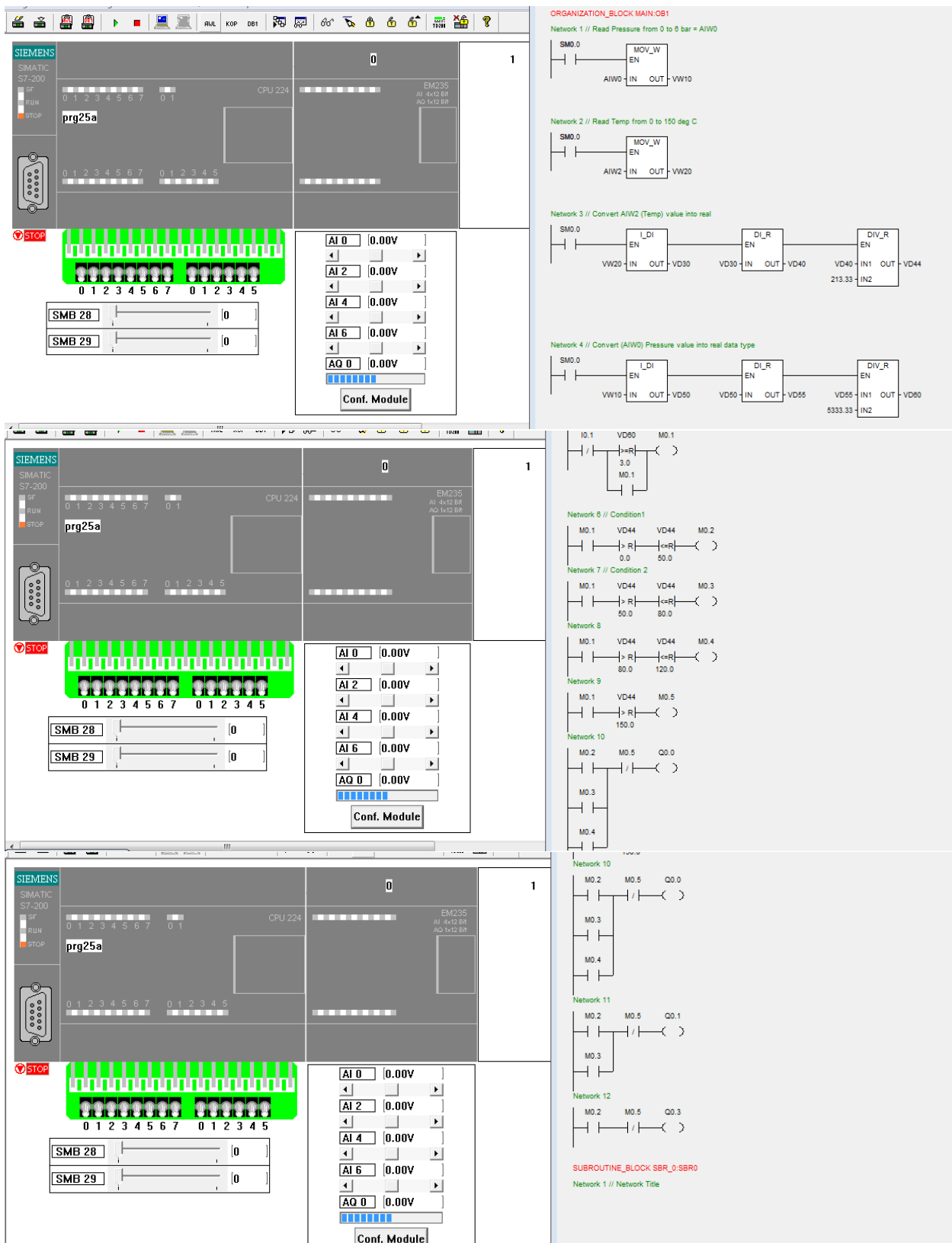


## Program #26

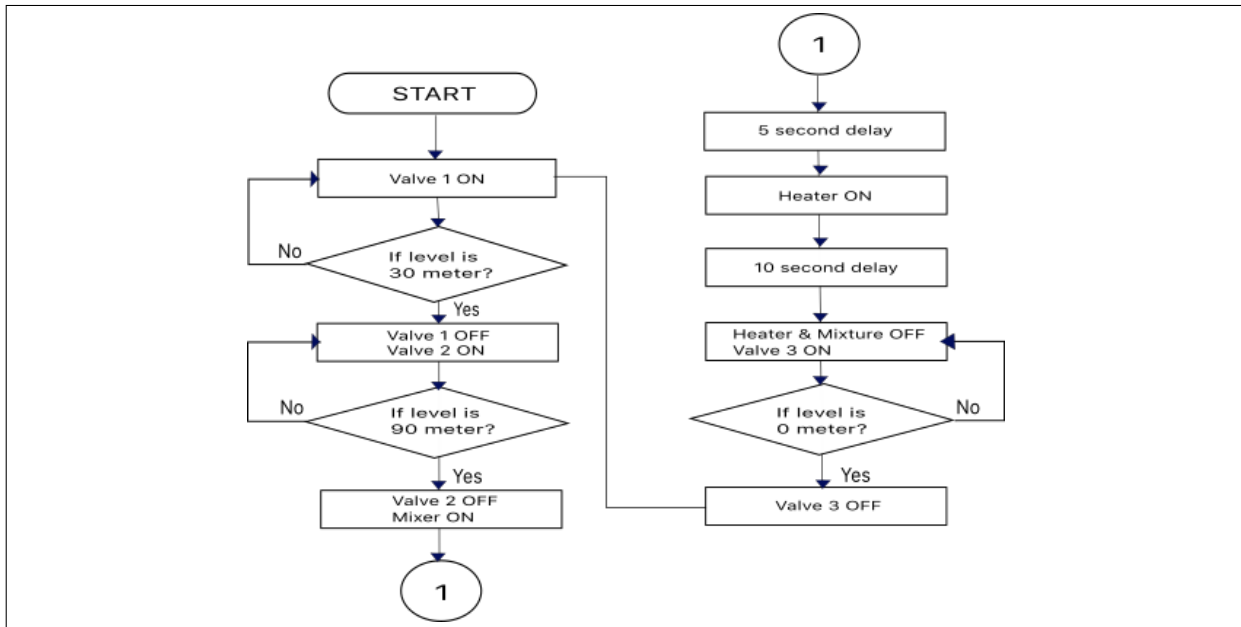


**Answer.**

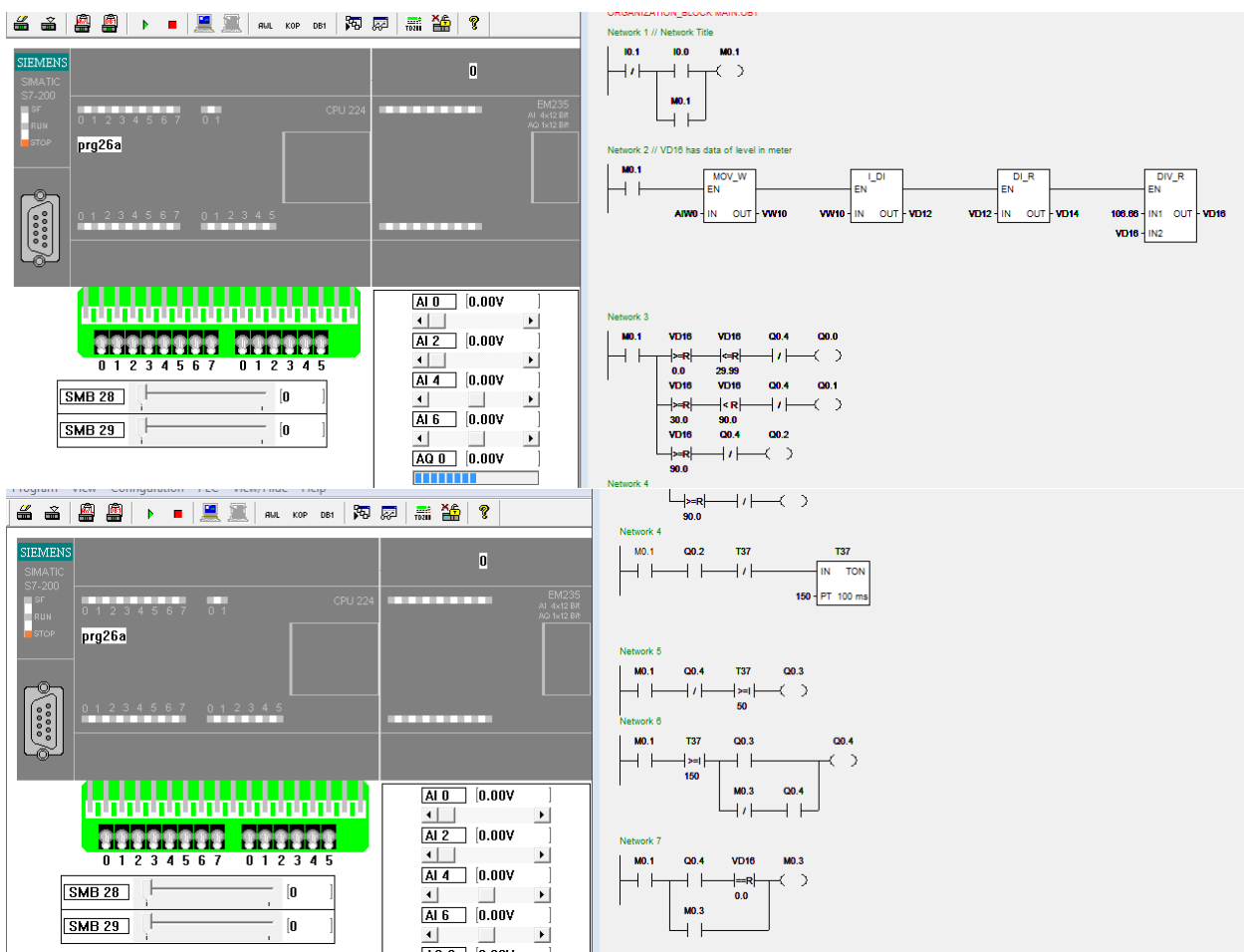

## Program #27

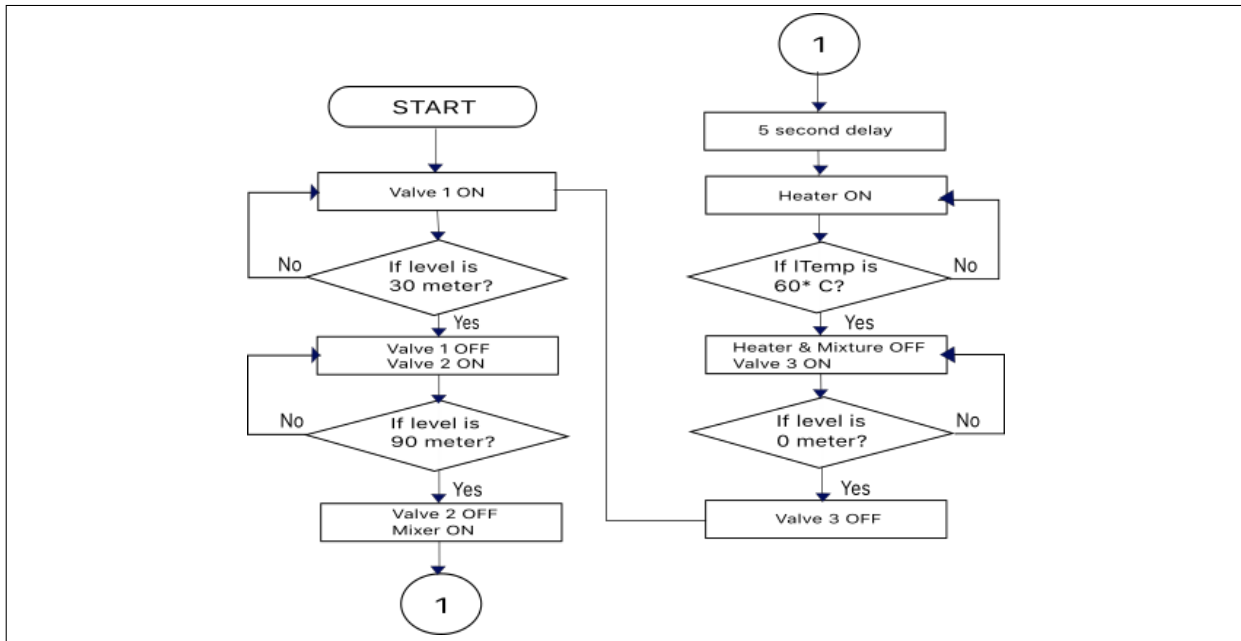


Answer.

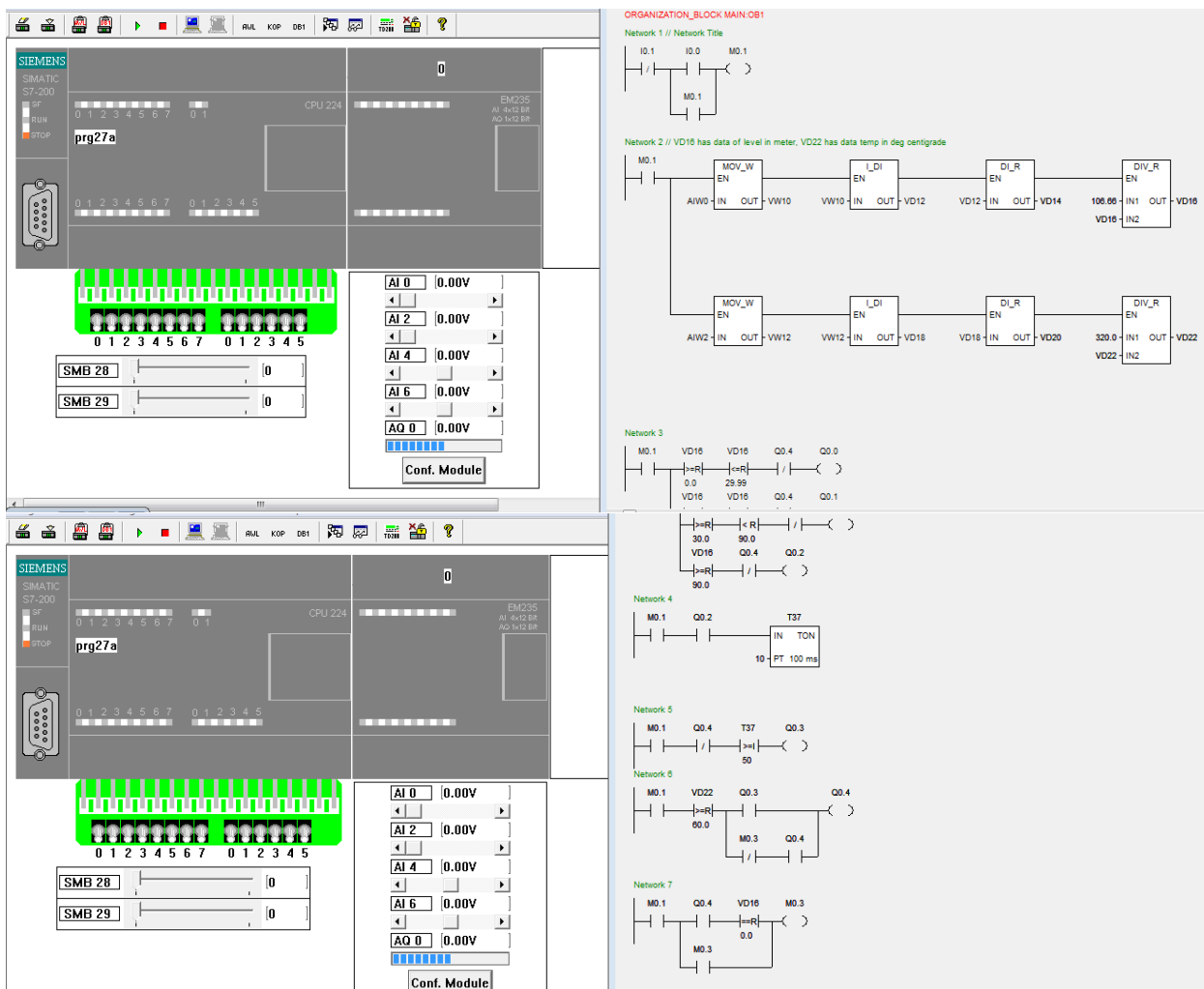


**Program #28**

There is one Induction motor with synchronous speed of 1500 RPM, so design a ladder logic in such a way that IM will start by increasing its speed in some discrete interval as shown in figure. where total time delay to achieve full load speed is 50 sec given.

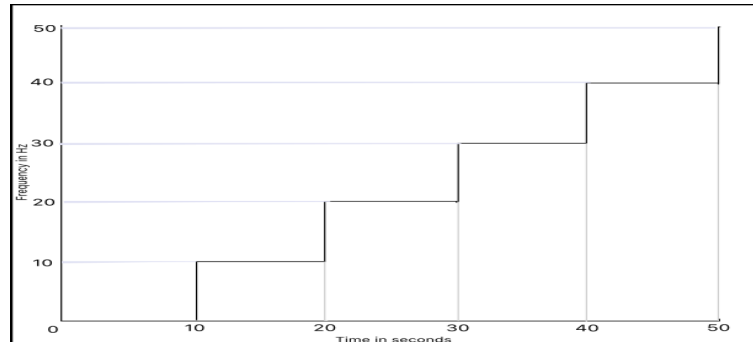
1. Increase speed in 5 such different discrete interval as shown in figure



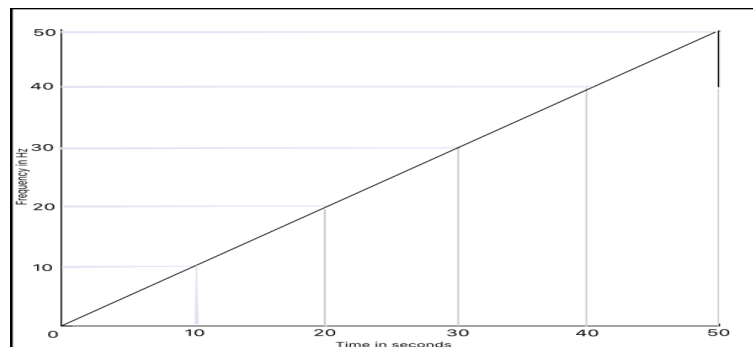2. design part(a) with different universal logic
3. increase speed in 50 such different discrete interval, or more fine linear increasing manner



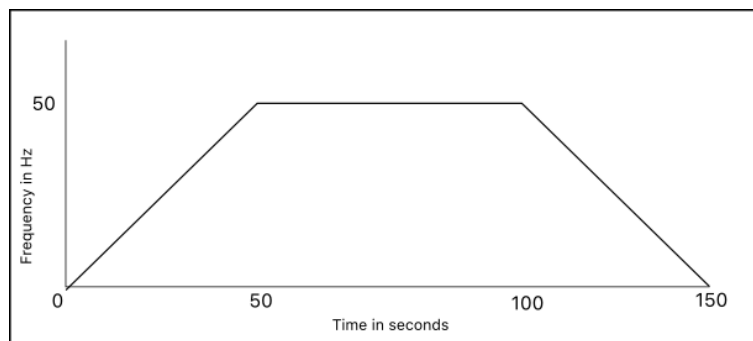
4. increase speed with 50 discrete levels in 50 sec and after 100 sec decrease speed with same levels in same time interval







Answer.

1.

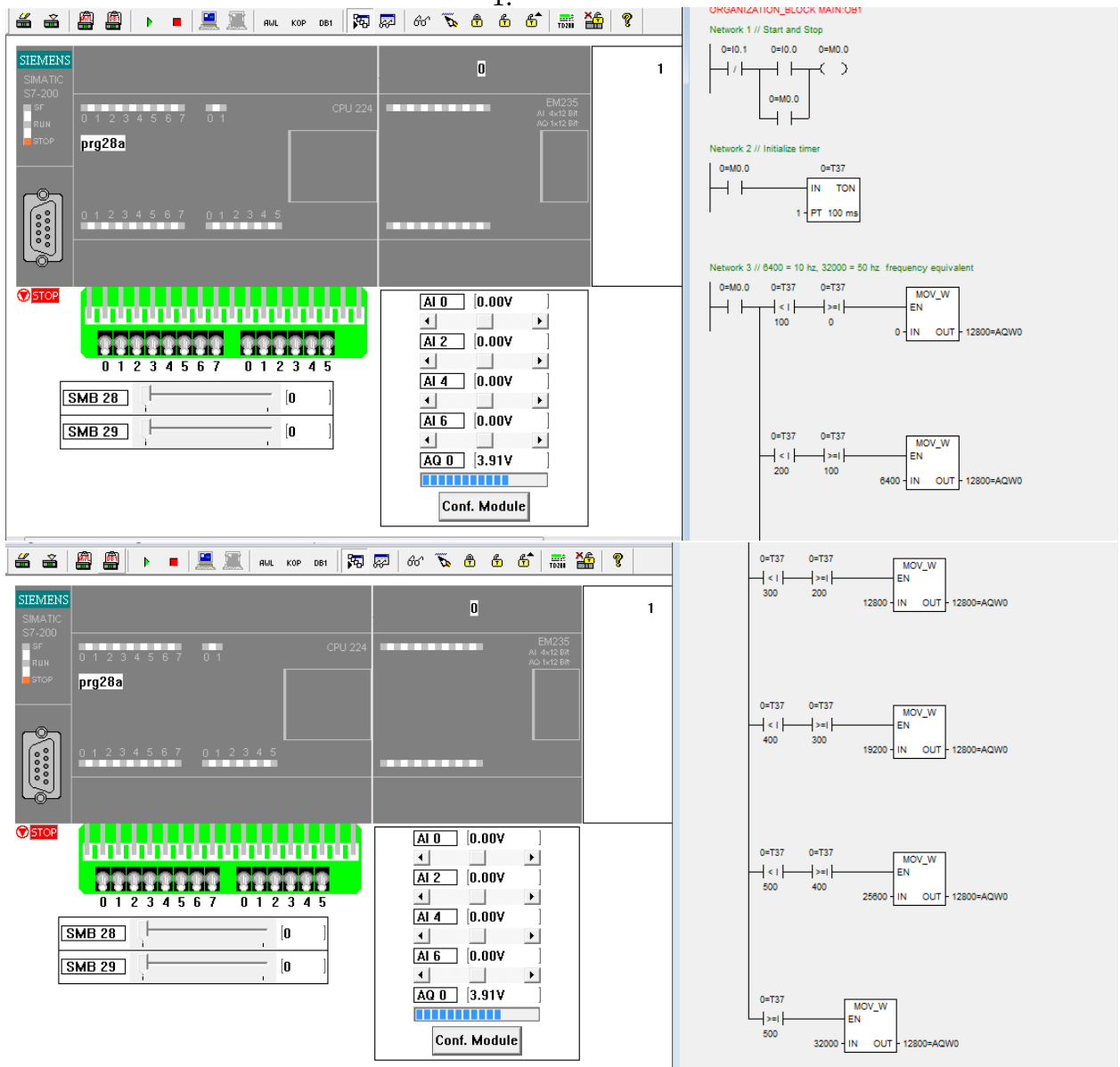


2.

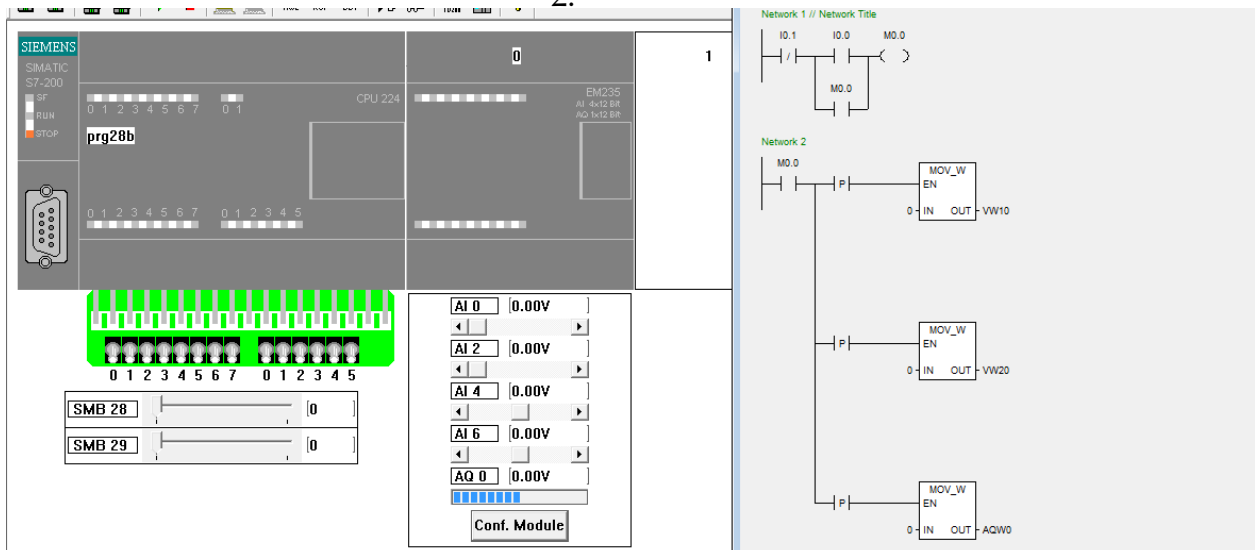

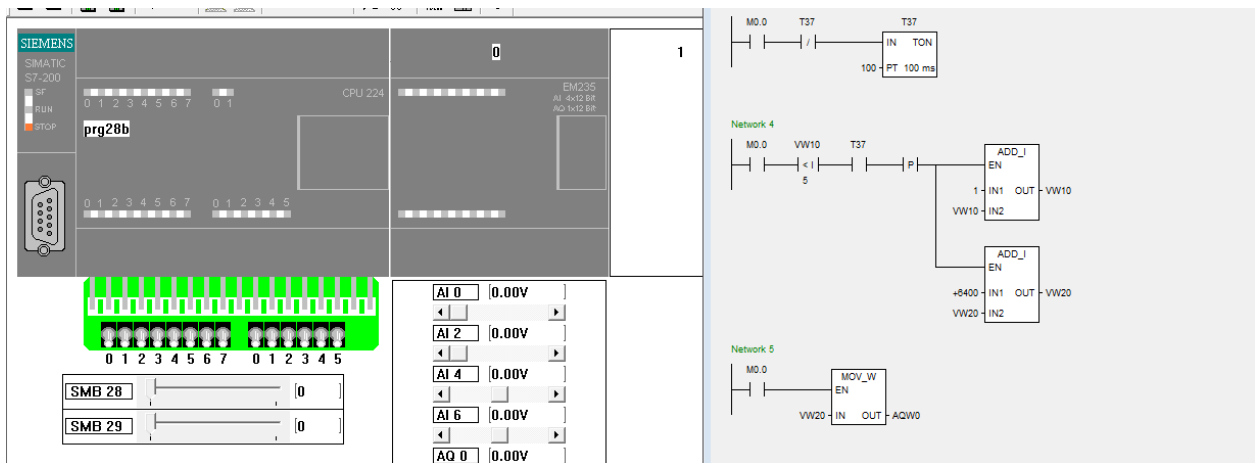

3.

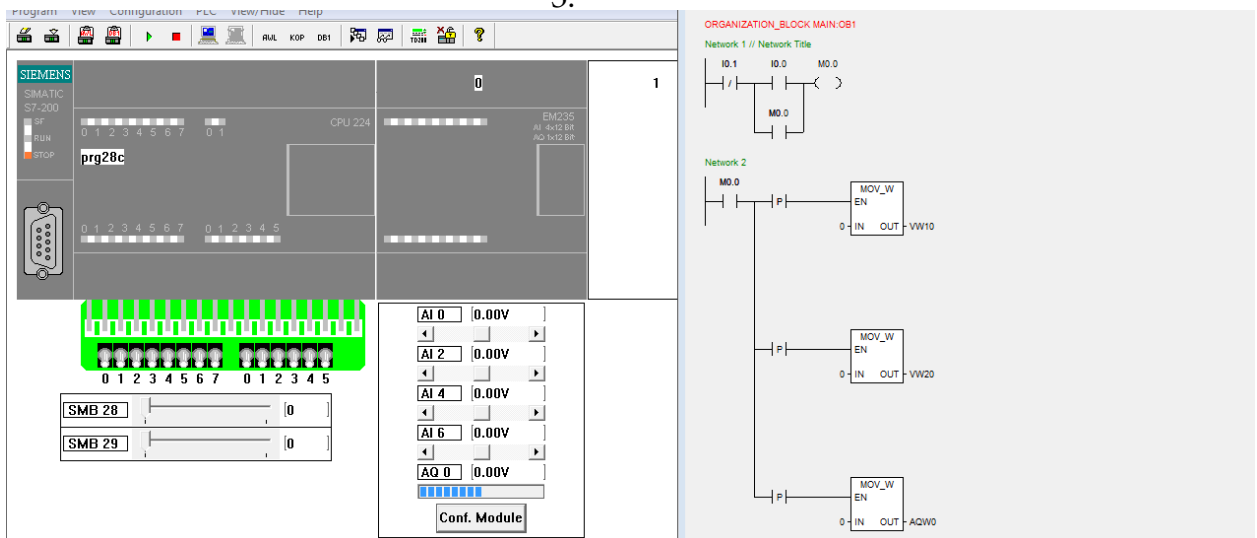

4.

